

Microphone Breakout Circuit

Materials Needed

- Feather M4 Express
- SparkFun Microphone Breakout
- 3 jumper wires
- Resistor (10k ohm)
- Power Source (Laptop or Battery)

Connections

1. 3V - VCC
2. GND - resistor - gnd (microphone)
3. A0 - AUD